

部分习题参考答案

第1章

1-1 (a) -15W (b) 12W (c) $-27\cos^2\omega t\text{W}$ (d) -9W

1-2 1) 10V 2) -2A 3) -1A 4) $-20\mu\text{W}$ 5) -1A 6) -10V 7) -1mA 8) -4mW

1-3 4V , 2A ; 1V , 8A

1-5 (a) 28Ω (b) 35V (c) -2A

1-6 -21.6W -14.4W ; -48W -75W

1-7 -72W -36W

1-8 均为 40V , 1A

1-9 (1) 5A (2) 1A , 4A , 4A , 6A , 2A (3) 8V , -10V , -18V

1-10 $-19/7\text{V}$, $1/7\text{A}$

1-11 6V , 6V , 0V

1-12 30V , 10A

1-13 2V , 2A

1-14 28V , 1A

1-15 (1) -10V , 25V , -7V , -8V

(2) -0.2A , 2.5A , -1A , -1A , -0.8A , -2.7A , 3.5A , 0

1-16 -4A , 8W , 16W , 6W , 20W , -50W

1-17 250W , -50W , -200W

1-18 50Ω , 1Ω

1-19 a) -48W , -30W , -150W , b) -180W , -300W , -1875W ,

1-20 1A 13A

1-21 5V 1V 2V

1-23 13V 10Ω

1-24 16W 电源

1-25 27W

1-26 3Ω

第2章

2-1 (a) 3Ω (b) 4.4Ω (c) 0.5Ω
(d) 1.269Ω (e) 3Ω (f) 1.448Ω

2-2 3Ω

2-3 1.5Ω $5/3\Omega$

2-4 (a) 30W , 0.125A ; (b) 720W , -1A

2-5 (1) $R_{ab} = 32\Omega$; (b) $R_{ab} = 12.15\Omega$, $I_{S1} = \frac{63}{13}\text{A}$, $I_{S2} = -\frac{9}{13}\text{A}$

2-6 8V 4V 2V 1V 即 $\frac{U_i}{2^n}$

2-7 1A , 5V ; 67.5V , 3A

2-8 (1) $U_1 = R_1 I_1 + U_2$, $I_1 = \frac{U_2}{R_2} + I_2$ (2) $U_2 = \frac{R_2}{R_1 + R_2} U_1$

2-9 (1) 400V (2) 363.6V -9.1%

2-10 $R_L = 40\Omega$, 加负载前 $P = 9.6\text{W}$, 加负载后 $P = 10.8\text{W}$

2-11 $R_2 = 80\Omega$, $R_3 = 20\Omega$, $R_4 = 16\Omega$

2-12 15V 0

2-13 $\frac{R_5}{R_8} = \frac{R_6}{R_9} = \frac{R_7}{R_{10}}$

2-14 三个 $\frac{100}{3}\Omega$ 电阻 Y 形联接的电路

2-15 (a) $I_{S1} - I_{S2}$ (b) I_{S2} (c) U_{S2}
(d) 42V 串 6Ω (e) 10V 串 5Ω (f) 1A 并 5Ω
(g) 8A 并 5Ω (h) 2A 并 4Ω (i) 1A 并 2Ω

2-16 (a) 10V 电压源 (b) 3A 并 2Ω (c) 1.2A 并 5Ω
(d) 3A 并 1Ω (e) 11V 串 50Ω (f) 5V 串 1Ω

2-17 6V , 2Ω ; 3A , 0.5S

2-18 (1) -5A (2) $\frac{10}{3}\text{A}$ (3) 1.455A 或 -11.455A

2-19 (a)8A (b)4A

2-20 $I = 0.375\text{A}$, 发出 112.5W

2-21 (a) 3Ω (b) 6Ω (c) 5Ω (d) 8Ω

2-22 (a) 59.991Ω (b) -1.2Ω (c) $\frac{18+12\mu}{9+2\mu}k\Omega$ (d) $-4k\Omega$

2-23 (a) $\frac{17}{43}$ (b) $\frac{4}{5}$

2-24 1A

2-25 (a) 8V (b) 2V

2-26 $U = \frac{2}{3}\text{V}$, 发出 $\frac{2}{9}\text{W}$

2-27 $I = -\frac{25}{12}\text{A}$

2-28 $U = 2\text{V}$, 分别发出 3W 、 336W 、 18W

2-29 -6Ω 6V 3A

第3章

3-1 4, 9, 28, 6, 3, 6

3-3 (a) $I_1=2\text{A}$, $I_2=3\text{A}$, $I_3=1\text{A}$ (b) $I_1=2\text{A}$, $I_2=1\text{A}$, $I_3=-3\text{A}$, $I_4=3\text{A}$

3-6 1A 18V

3-7 $I = 0.375\text{A}$, 发出 3.52W

3-9 2A 、 1A 、 3A 电流源发出的功率分别为 12W 、 -8W 、 -69W

3-10 $U = 10\text{V}$, $P = -11\text{W}$

3-11 $\frac{R + R_2}{4R + 2R_1 + 2R_2}$

3-12 1V 6V 3V -20V

3-14 8V

3-16 (a) 5V , 6V , 11V (b) -15V , -5V

3-18 $I = 2.5\text{A}$, $P_{5\text{A}} = -100\text{W}$

$$3-19 \quad U = \frac{24}{7} \text{V}, \quad I = \frac{1}{7} \text{A}, \quad P_{2U} = -\frac{192}{7} \text{W}, \quad P_{4I} = \frac{64}{49} \text{W}$$

$$3-22 \quad P_{20V} = 0.48 \text{W}$$

$$3-23 \quad I = 2 \text{A}, \quad U = 6 \text{V}$$

$$3-24 \quad I = 0.5 \text{A}, \quad P = -27.75 \text{W}$$

$$3-25 \quad 3 \text{W} \quad -14 \text{V} \quad -2 \text{W} \quad 3 \text{W}$$

$$3-27 \quad -56 \text{W} \quad -3 \text{W}$$

$$3-28 \quad 4 \Omega$$

$$3-29 \quad -1 \text{A}$$

$$3-30 \quad -817 \text{W}$$

第 4 章

$$4-1 \quad (\text{a}) 2 \text{A} \quad (\text{b}) -2 \text{A}$$

$$4-2 \quad u(t) = 20 \sin t - e^{-t} \text{V}$$

$$4-3 \quad \frac{R_4 u_{s2}}{R_2 + R_4} + \frac{R_2 R_3 - R_1 R_4}{(R_1 + R_3)(R_2 + R_4)} u_{s2}$$

$$4-4 \quad -11.5 \text{V} \quad -1.5 \text{V} \quad 1 \text{V} \quad -2 \text{V} \quad -2 \text{V}$$

$$4-5 \quad 3 \text{V}$$

$$4-6 \quad 84 \text{W}, 150 \text{W}$$

$$4-7 \quad (1) 300 \text{V} \quad (2) 348 \text{V}$$

$$4-8 \quad 3$$

$$4-9 \quad -36 \text{V}, 144 \text{W}$$

$$4-10 \quad (2) 18 \text{V} \text{ 上正下负} \quad (3) 5 \text{A} \text{ 由上向下流}$$

$$4-11 \quad 6.4 \Omega$$

$$4-12 \quad 1.5 \Omega$$

$$4-13 \quad (\text{a}) 14 \text{V}, 15 \Omega \quad (\text{b}) 16 \text{V}, 16 \Omega \quad (\text{c}) 14600 \text{V}, 210 \Omega$$

$$(\text{d}) 0 \text{V}, 7 \Omega \quad (\text{e}) 12 \text{V}, 4.5 \Omega \quad (\text{f}) -2 \text{V}, -1 \Omega$$

4-14 $U_{oc} = 20V$, $R_{eq} = 2.083\Omega$

4-15 (a) 1Ω , $4W$ (b) $\frac{21}{16}\Omega$, $\frac{12}{7}W$ (c) 8Ω , $2W$ (d) 4Ω , $4W$

4-16 $R_L = 2.5\Omega$ 或 $R_L = 22.5\Omega$

4-17 (1) $R_L = \frac{125}{6}\Omega$, $P_{max} = 235.2W$; (2) 26.64% ; (3) $857.6W$; (4) $-4.04W$

4-18 8Ω

4-19 $1 + \frac{R_1 R_{S1}}{R_2 (R_1 + R_{S1})}$

4-20 (1) 5Ω , $125W$

(2) 并联 $IS=10A$ 的电流源, 方向为由节点 1 指向节点 0

(3) 20Ω

4-21 $54V$

4-22 $1.6V$

4-23 $2A$

4-24 (1) $\frac{1}{3}A$ (2) $\frac{3}{2}V$

4-25 (1) 15Ω (2) -1 (3) 3.75Ω 2.5Ω (4) 12.5Ω

4-26 (1) 6Ω (2) 2 (3) 18Ω 6Ω 3Ω

4-28 是

4-30 $U_o = -\beta \frac{R_L \frac{\frac{U_{s1}}{R_1} + \frac{U_{s2}}{R_2} + \frac{U_{s3}}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}}{R_4}$, 反向加法运算

4-31 $2.25V$ $1.6A$

4-32 $3.6V$

4-33 $10mA$

$$4-36 (2) \quad L_0 = \frac{-U_1 L + \sqrt{U_1 U_2 L^2 - \frac{(U_2 - U_1)^2 RL}{2r}}}{U_2 - U_1}$$

$$(3) \quad U=866.6\text{V}, \quad L_0=15.5\text{km}$$

$$4-37 \quad 3\text{A}$$

$$4-38 \quad 6\text{V}$$

$$4-39 \quad 8.86\text{W}$$

第 5 章

$$5-1 \quad 1.8\text{mA}$$

$$5-2 \quad 6\text{V}$$

$$5-3 \quad 10\text{k}\Omega$$

$$5-4 \quad -R$$

$$5-5 \quad \frac{1}{2}$$

$$5-7 \quad 2.5\text{k}\Omega \quad 1\text{k}\Omega$$

$$5-8 \quad u_0 = -\frac{G_3 G_1}{G_2(G_1 + 2G_3)} u_s$$

$$5-9 \quad \frac{35}{4} \text{mV}$$

$$5-10 \quad \text{设 } G_k = \frac{1}{R_k}, \frac{-G_1 G_4}{(G_1 + G_2 + G_3 + G_4)G_5 + G_3 G_4}$$

$$5-11 \quad \frac{G_1 G_2}{G_2(G_1 + G_4) + G_5(G_1 + G_2 + G_3 + G_4)}$$

$$5-12 \quad \cos 5t \text{mA}$$

$$5-13 \quad -1$$

$$5-14 \quad u_o = 18(u_2 - u_1)$$

$$5-15 \quad R$$

$$5-16 \quad u_o = u_{s1} - u_{s2}$$

$$5-17 \quad R_L = 1\text{K} \quad P_{\max L} = 1\text{mw}$$

第6章

6-2 (a) $u_{C1}=5\text{V}$, $i_{C1}=\frac{4}{3}\text{A}$, $u_{C2}=10\text{V}$, $i_{C2}=1\text{A}$

(b) $u_C=15\text{V}$, $i_C=-\frac{1}{6}\text{A}$

6-3 (a) $i_L=2\text{A}$, $u_L=-80\text{V}$, $u_C=6\text{V}$, $i_C=-0.6\text{A}$, $i_L=0.1\text{A}$, $u_L=-6\text{V}$

6-4 (a) (1) $i_{L1}=i_{L2}=20\text{A}$, $u_{C1}=40\text{V}$, $u_{C2}=20\text{V}$, $u_{L1}=20\text{V}$, $u_{L2}=-20\text{V}$, $i_{C1}=i_{C2}=0$

(2) $i_{L1}=i_{L2}=20\text{A}$, $u_{C1}=20\text{V}$, $u_{C2}=40\text{V}$, $u_{L1}=u_{L2}=0$, $i_{C1}=i_{C2}=0$

(b) (1) $i_{L1}=1\text{A}$, $i_{L2}=-2\text{A}$, $u_C=6\text{V}$, $u_{L1}=-14\text{V}$, $u_{L2}=0\text{V}$, $i_C=0$

(2) $i_{L1}=-2.5\text{A}$, $i_{L2}=-2\text{A}$, $u_C=6\text{V}$, $u_{L1}=u_{L2}=0$, $i_C=0$

6-5 $u_C(t)=40\text{e}^{-t}\text{V}$, $i(t)=0.2\text{e}^{-t}\text{mA}$

6-6 $i_L(t)=-6\text{e}^{-t}\text{A}$

6-7 $0.24(\text{e}^{-500t}-\text{e}^{-1000t})\text{A}$, $0.4+0.24(\text{e}^{-500t}-\text{e}^{-1000t})\text{A}$

6-8 $10\mu\text{F}$, 2.2A , $110(1\text{A}$

6-9 $\tau=2RC$, $u_C(t)=I_s R(1-\text{e}^{-\frac{t}{\tau}})$, $p(t)=-0.5I_s^2 R(2-\text{e}^{-\frac{t}{\tau}})\text{W}$

6-10 $\tau=\frac{2L}{R}$, $i_L(t)=\frac{U_s}{R}(1-\text{e}^{-\frac{t}{\tau}})\text{A}$, $p(t)=-0.5\frac{U_s^2}{R}(2-\text{e}^{-\frac{t}{\tau}})\text{W}$

6-11 $i=\frac{1}{5}(1-\text{e}^{-5t})\text{A}$

6-12 $i=0.5(1-\text{e}^{-5t})\text{A}$

6-13 $i=0.5+\frac{53}{14}\text{e}^{-3t}\text{A}$

6-14 $u_C=8-16\text{e}^{-0.25t}\text{V}$

6-15 $i_L=\begin{cases} 4-4\text{e}^{-10^3 t}\text{mA} & 0\leq t\leq 5\text{ms} \\ 4\text{e}^{-500t}\text{mA} & t>5\text{ms} \end{cases}$ $u=\begin{cases} 8-4\text{e}^{-10^3 t}\text{V} & 0\leq t\leq 5\text{ms} \\ 6\text{e}^{-500t}\text{V} & t>5\text{ms} \end{cases}$

6-16 $i_L=(7-6\text{e}^{-t})\text{A}$, $i_R=3\text{e}^{-t}\text{A}$

6-17 $u_C=(14+16\text{e}^{-\frac{25}{3}t})\text{V}$, $i=(0.2+0.8\text{e}^{-\frac{25}{3}t})\text{mA}$

$$6-18 \quad u_C = (16 - 9e^{-\frac{1}{6}t})V, \quad i_L = 1 - 0.75e^{-2t}A$$

$$6-19 \quad i_L = \begin{cases} 1.5e^{-1.5 \times 10^5 t} \text{ mA} & 0 \leq t \leq 10\mu s \\ 1.5 - 1.165e^{-\frac{15}{7} \times 10^5 t} \text{ mA} & t \geq 10\mu s \end{cases}$$

$$6-20 \quad \tau = 2.4 \times 10^{-6} \text{ s} \quad u_C = (-1.6 - 0.4e^{\frac{t}{\tau}})V, \quad i_C = \frac{1}{6}e^{\frac{t}{\tau}}A, \quad i = (8 - \frac{2}{15}e^{\frac{t}{\tau}})A,$$

$$6-21 \quad \tau = \frac{1}{130} \text{ s}, \quad i_L = (\frac{1}{13} - \frac{3}{26}e^{\frac{t}{\tau}})A \quad u = \frac{4}{13} - \frac{6}{13}e^{\frac{t}{\tau}}V$$

$$6-22 \quad (1) \quad [-42.55e^{-125t} + 81.37\sqrt{2}\cos(314t - 68.3^\circ)]V$$

$$(2) \quad [-309.91e^{-5000t} + 219.57\sqrt{2}\cos(314t - 3.6^\circ)]V$$

$$6-23 \quad [-0.573e^{-250t} + 2.74\sqrt{2}\cos(314t - 81.5^\circ)]A$$

$$6-24 \quad u_C = (8 - 3e^{\frac{2t}{3}})V, \quad i = (\frac{2}{3}e^{\frac{2t}{3}} - 1)A$$

$$6-25 \quad u_C = (35 - 5e^{\frac{t}{3}})V \quad u_s = -20 - 10e^{-20t} + \frac{10}{3}e^{\frac{t}{3}}V$$

$$6-26 \quad u_C = (7.5 - 1.5e^{\frac{t}{2}})V \quad i = (\frac{15}{16} + \frac{3}{64}e^{\frac{t}{2}})A$$

$$6-27 \quad i_L = 4 - e^{-2t}A \quad i = 2 + 0.5e^{-2t}A$$

$$6-28 \quad (a) \quad i = [\varepsilon(t-1) + 2\varepsilon(t-2) - 3\varepsilon(t-3)]A$$

$$(b) \quad u = [2\varepsilon(t-t_0) - 2\varepsilon(t-2t_0)]V$$

$$(c) \quad i = [2\varepsilon(t) - 4\varepsilon(t-1) + 2\varepsilon(t-2)]A$$

$$(d) \quad u = [\varepsilon(t) - 3\varepsilon(t-2) + 2\varepsilon(t-3)]V$$

$$6-29 \quad (0.625 - 0.125e^{-t})\varepsilon(t)V$$

$$6-30 \quad i_L = (3 - 2e^{-t})A$$

$$6-31 \quad u_C = 19 - 7e^{\frac{t}{8}}V$$

$$6-32 \quad (1) \quad S_C(t) = 15(1 - e^{\frac{t}{3}})V$$

$$(2) \quad u_C = [150(1 - e^{-\frac{t}{3}})\varepsilon(t) - 300(1 - e^{-\frac{t-1}{3}})\varepsilon(t-1) + 150(1 - e^{-\frac{t-2}{3}})\varepsilon(t-2)]V$$

$$6-33 \quad (1) \quad \tau = 0.5\mu s \quad (2) \quad \tau = 6\mu s$$

$$u_o = [10e^{-\frac{t}{\tau}}\varepsilon(t) - 10e^{-\frac{t-6}{\tau}}\varepsilon(t-6) + 10e^{-\frac{t-12}{\tau}}\varepsilon(t-12) - 10e^{-\frac{t-18}{\tau}}\varepsilon(t-18) + 10e^{-\frac{t-24}{\tau}}\varepsilon(t-24) - 10e^{-\frac{t-30}{\tau}}\varepsilon(t-30)]V$$

$$6-34 \quad (1) \quad i_1 = (0.4 - 1.4e^{-2.5t})A, \quad i_2 = 0.7e^{-2.5t}A$$

$$(2) \quad i_1 = [(0.2 - 1.2e^{-2.5t})\varepsilon(t) + 0.2[1 - e^{-2.5(t-1)}]\varepsilon(t-1) - 0.4[1 - e^{-2.5(t-2)}]\varepsilon(t-2)]A$$

$$6-35 \quad i_L(t) = \frac{3}{5}\varepsilon(t) + \frac{2}{15}(1 - e^{-10t})\varepsilon(t) - \frac{2}{5}[1 - e^{-10(t-1)}]\varepsilon(t-1) + \frac{2}{15}(1 - e^{-10(t-3)})\varepsilon(t-3)A$$

$$6-36 \quad (1) \quad i_L = e^{-2t}\varepsilon(t)A, \quad (2) \quad i_L = (e^{-t} - e^{-2t})A$$

$$(3) \quad i_L = \left[\left(\frac{t}{2} + \frac{1}{4}e^{-2t} - \frac{1}{4}\right)\varepsilon(t) - \left(\frac{t-1}{2} + \frac{1}{4}e^{-2(t-1)} - \frac{1}{4}\right)\varepsilon(t-1)\right]A$$

$$6-37 \quad 8.22 \times 10^6 e^{-5 \times 10^4 t} \sin(3.04 \times 10^5 t)]A, \quad 6.43 \times 10^6 A, \quad 4.63\mu s$$

$$6-38 \quad u_C = \frac{200}{3}(e^{-200t} - e^{-50t})V$$

$$6-39 \quad u_C = 188.15e^{-10t}\sin(49.97t - 71.19^\circ)V, \quad i_L = -0.96e^{-10t}\sin(49.97t + 7.94^\circ)A$$

$$6-40 \quad u_C = (14e^{-2t} - 10e^{-3t})V$$

$$6-41 \quad u_L = -309.85e^{-250t}\sin 12908tV,$$

$$6-42 \quad i_L = (5 - 500te^{-200t})A$$

第7章

7-1 (1) $A_1 = 2\sqrt{2}\angle 45^\circ$; (2) $A_2 = 5\angle -37^\circ$; (3) $A_3 = 5\angle 90^\circ$;

(4) $A_4 = 6\angle 90^\circ$; (5) $A_5 = 10\angle 0^\circ$; (6) $A_6 = 2\angle 60^\circ$ 。

7-2 (1) $B_1 = 4 + j3$; (2) $B_2 = 5 + j5\sqrt{3}$; (3) $B_3 = -j8$;

(4) $B_4 = \sqrt{2} + j\sqrt{2}$; (5) $B_5 = 7$; (6) $B_6 = -3$ 。

7-3 (1) 220V, 50Hz, 0.02s

(2) $\dot{U}_1 = 220\angle 120^\circ \text{ V}$, $\dot{U}_2 = 220\angle -120^\circ \text{ V}$, $\varphi = \psi_{u1} - \psi_{u2} = -120^\circ$

7-4 $i(t) = 5\cos(314t + 60^\circ) \text{ V}$, 2.5A, -2.5A

7-5 (1) 0.02s, 50Hz, 110V, 20A

(2) $u(t)$ 超前 $i(t)$ 180°

7-6 $220\angle 90^\circ \text{ V}$, $220\sqrt{3}\angle 0^\circ \text{ V}$

7-7 (1) $20\sqrt{2}\cos(1000t + 60^\circ) \text{ V}$

(2) $1.25\sqrt{2}\cos(1000t - 30^\circ) \text{ V}$

(3) $2\sqrt{2}\cos(1000t + 150^\circ) \text{ V}$

7-8 (1) a) 50V, b) $50\sqrt{2} \text{ V}$

(2) a) 50V, 0, b) 0, 0, 50V

7-9 5A

7-10 都有可能, 谐振

7-11 (1) 36.87° , 10V (2) -143.13° , 0

7-12 $u_R(t) = 100\cos 100t \text{ V}$, $u_L(t) = 100\cos(100t + 90^\circ) \text{ V}$

$u_C(t) = 200\cos(100t - 90^\circ) \text{ V}$, $u(t) = 100\sqrt{2}\cos(100t - 45^\circ) \text{ V}$

7-13 $i_R(t) = 100\cos 100t \text{ A}$, $i_L(t) = 10\cos(100t - 90^\circ) \text{ A}$

$i_C(t) = 5\cos(100t + 90^\circ) \text{ A}$, $i(t) = 11.18\cos(100t - 26.57^\circ) \text{ A}$

7-14 $200\cos(1000t + 45^\circ)\text{V}$

7-15 $3\sqrt{2}\cos(10t + 113.13^\circ)\text{A}$

7-16 (1) 0

(2) $380\sqrt{2}\cos 314t\text{V}$, $380\sqrt{2}\cos(314t - 120^\circ)\text{V}$, $380\sqrt{2}\cos(314t + 120^\circ)\text{V}$

7-17 (1) $0.4\angle 98.13^\circ\text{A}$, $\angle 98.13^\circ\text{V}$, $\angle 8.13^\circ\text{V}$

(2) $0.4\sqrt{2}\cos(1000t + 98.13^\circ)\text{A}$, $60\sqrt{2}\cos(1000t + 98.13^\circ)\text{V}$,

$80\sqrt{2}\cos(1000t + 8.13^\circ)\text{V}$

(3) $\varphi = \psi_{u_{ab}} - \psi_{u_{bc}} = 90^\circ$

7-18 $\frac{1}{\omega C} = 5\Omega$, $35\angle 66^\circ\text{V}$

7-19 $i_C(t) = 2\sqrt{2}\cos(\omega t + 180^\circ)\text{A}$

$i_L(t) = 10\cos(\omega t + 155.4^\circ)\text{A}$

$u(t) = 635\sqrt{2}\cos(\omega t + 107^\circ)\text{V}$

7-20 $5\sqrt{2}\angle -135^\circ\text{V}$

第 8 章

8-1 22Ω , $110\sqrt{2}\cos(314t - 15^\circ)\text{V}$, $190.5\sqrt{2}\cos(314t + 75^\circ)\text{V}$

8-2 $0.318\mu\text{F}$, $22\cos(100\pi t + 45^\circ)\text{mA}$, $22\cos(100\pi t - 45^\circ)\text{V}$

8-3 电容 $C = \frac{\sqrt{3}}{300R}$

R 单位为 Ω , C 单位为 F

8-4 (1) 3Ω , 0.4H (2) $13.42\cos(15t + 26.57^\circ)\text{V}$

8-5 (1) -5Ω , $10 + \text{j}10\Omega$ (2) $10 - \text{j}10\Omega$, 电压滞后电流 45°

8-6 $\dot{I}_R = 2.5\angle 45^\circ\text{A}$, $\dot{I}_L = 3.33\angle -45^\circ\text{A}$, $\dot{I}_C = 4.17\angle -8.31^\circ\text{A}$,

$$\dot{U}_C = 25 \angle -98.31^\circ \text{V}, \quad \dot{U}_S = 18 \angle -78.92^\circ \text{V}$$

8-9 (1) $10 \angle 0^\circ \Omega$, $0.1 \angle 0^\circ \text{S}$, 500W , 0 , 500VA

(2) $10 \angle -30^\circ \Omega$, $0.1 \angle 30^\circ \text{S}$, 433W , -250var , 500VA

(3) $4 \angle 90^\circ \Omega$, $0.25 \angle -90^\circ \text{S}$, 0 , 50var , 50VA

(4) $10 \angle 60^\circ \Omega$, $0.1 \angle -60^\circ \text{S}$, 62.5W , 108.25var , 125VA

8-10 $R = 20\Omega$, $Q = 560\text{Var}$

8-11 $R = 10\sqrt{3}\Omega$, $X_C = -60\Omega$, $\dot{U}_S = 240 \angle 0^\circ \text{V}$

8-12 $I_1 = 2\sqrt{2}\text{A}$, $I_2 = 10\text{A}$, $Z_1 = 50 + j50\Omega$, $Z_2 = 12 - j16\Omega$

8-13 $R_2 = 15.8\Omega$, $L = 48.76\text{mH}$, $\cos\varphi = 0.97$, $P = 6.42\text{kW}$

8-14 $68.76\mu\text{F}$

8-15 (1) 21.26A , 3960W , 0.8466

(2) 22.49Ω , 6112W , 0.9261

(3) $57.85\mu\text{F}$

8-16 $C = 37\mu\text{F}$

8-17 $R = 10\sqrt{3}\Omega$, $U = 80\sqrt{3}\text{V}$, $P = 240\sqrt{3}\text{W}$, $Q = -240\text{Var}$, $S = 480\text{VA}$

8-18 $X_L = 9.6\Omega$, $X_C = -15\Omega$

8-19 (1) $i_{R1}(t) = i_{L1}(t) = \sqrt{2} \cos(100t - 36.87^\circ) \text{A}$

(2) $i_{L2}(t) = 0.6\sqrt{2} \cos(100t - 36.87^\circ) \text{A}$

(3) $i_C(t) = 0.6\sqrt{2} \cos(100t + 143.13^\circ) \text{A}$

8-20 $Z = 10 \angle 16.2^\circ = 9.6 + j2.8\Omega$, $X_L = 20\Omega$, $X_C = -40\Omega$, $P = 1200\text{W}$

8-21 $R = 8\Omega$, $X_L = 8\sqrt{3}\Omega$, $X_C = -4\sqrt{3}\Omega$, $I_2 = 2.5\text{A}$

8-22 366Ω

8-23 5mH

8-24 15.6V, 0.234

8-25 $\frac{CR_2}{R_1}, \frac{RR_1}{R_2}$

8-26 $(\omega L)^2 - \frac{2L}{C} + R^2 = 0$, 其中一特例 $\omega = \sqrt{\frac{1}{LC}}, R = \sqrt{\frac{L}{C}}$

8-27 $\omega^2 = \frac{1}{2LC}$

8-28 (1) $1\angle 0^\circ \Omega, \frac{\sqrt{2}}{2}\angle -45^\circ$

(2) $10\angle 0^\circ \text{A}, 2.5\sqrt{2}\angle -135^\circ \text{V}$

8-29 $\omega RC = 1$

8-31 $\omega^2 LC = 2$, $\dot{U}_C$ 由与 $\dot{U}_s$ 同相变至反相

8-33 a) $\dot{U}_{oc} = \frac{R_3 j\omega L}{(R_1 + R_2)R_3 + j\omega L(R_1 + R_2 + R_3)} \dot{U}_s$

$$Z_{eq} = \frac{[R_1 + (1 + \alpha)R_2]R_3 j\omega L}{(R_1 + R_2)R_3 + j\omega L(R_1 + R_2 + R_3)}$$

b) $\dot{U}_{oc} = \frac{(j\omega C_2 - g_m)}{-\omega^2 C_1 C_2 + j\omega C_2(C_1 + g_m)} \dot{I}_s$

$$Z_{eq} = \frac{C_1 + j\omega(C_1 + C_2)}{-\omega^2 C_1 C_2 + j\omega C_2(C_1 + g_m)}$$

8-34 $u_C(t) = 7.9 \cos(10^3 t + 108.4^\circ) \text{V}$

8-35 $i_1(t) = 1.37 \cos(10^3 t + 16^\circ) \text{A}$

8-36 $1.434\angle 125.54^\circ \text{V}, 0.6\angle -146.31^\circ \text{V}, 1.54\angle 102.53^\circ \text{A}$

8-37 $4.16\angle 3.48^\circ \text{A}$

8-38 $1.2 + j0.6\Omega, 0.165 \text{W}$

8-39 $4 + j3\Omega, 2.25 \text{W}$

$$8-40 \quad Z_L = 20\Omega, \quad P_{\max} = 7.8125\text{W}$$

$$8-41 \quad 2\angle 0^\circ \Omega, \quad 4.5\text{W}, \quad 4 \text{ 倍}$$

$$8-42 \quad (1) \quad P = 105\text{W} \quad (2) \quad P_{\max} = 12.5\text{W}$$

$$8-43 \quad -\frac{500}{j\omega + 1000}$$

$$8-44 \quad Z_i = j\omega R^2 C \quad \text{电感值为 } R^2 C$$

$$8-45 \quad 10\Omega, \quad 10\text{mH}, \quad 2.5$$

$$8-46 \quad R = 6\Omega \quad L_2 = \frac{100}{3}\text{mH}$$

$$8-47 \quad R_1 = R_2 = 5\sqrt{3}\Omega, \quad X_{L_1} = X_{L_2} = 5\Omega, \quad X_C = -10\Omega$$

$$8-48 \quad I_R = 5\text{A}, \quad I_L = I_C = 2\text{A}$$

$$8-49 \quad R = 2\Omega, \quad C_2 = 440\mu\text{F}$$

$$8-50 \quad R_1 = \omega L = 25\Omega$$

$$8-51 \quad \omega = \frac{1}{RC} \Rightarrow f = \frac{1}{2\pi RC}$$

$$8-52 \quad (1) \quad 5.24\Omega, \quad 0.278\text{mH}, \quad 150, \quad \text{此时 } U_1 \text{ 值最小}$$

$$(2) \quad 230\text{pF}$$

$$8-53 \quad (1) \quad L = 0.07\text{H}, \quad C = 145\mu\text{F}$$

$$(2) \quad u_L(t) = 330\sqrt{2} \cos(314t - 159^\circ)\text{V}$$

$$8-54 \quad i_1 = 2 \cos(1000t - 45^\circ)\text{A}$$

$$i_2 = \sqrt{2} \cos(1000t + 90^\circ)\text{A} = i_3$$

$$P = 100\text{W}$$

第9章

9-1 a) $1-2'$ b) $1-2$ c) $1-2$

d) $1-2'$, $1-3'$, $2-3'$ e) $1-2$, $1-3'$, $2'-3'$

9-3 21.17mH

9-4 0.1H

9-5 (1) 100.30V, 120.05V (2) 625μF

9-6 设 $\dot{U}_s = 220\angle 0^\circ \text{V}$, $\dot{I}_1 = 2.96\angle -61.13^\circ \text{A}$

$\dot{I}_2 = 2.504\angle -106.88^\circ \text{A}$, $\dot{I}_3 = 2.16\angle -5.27^\circ \text{A}$

9-7 $\dot{I}_1 = \dot{I}_2 = \sqrt{2}\angle -45^\circ \text{A}$, $\dot{I}_3 = 0$, $\dot{U}_{L1} = 50\sqrt{2}\angle 45^\circ \text{V}$

9-8 $1.51\angle 34.2^\circ \text{A}$

9-9 $5\angle 0^\circ \text{V}$

9-11 0.01H

9-12 1.67H

9-13 $\dot{I} = 5\sqrt{2}\angle 45^\circ \text{A}$, $\dot{I}_1 = \angle 90^\circ \text{A}$, $\dot{I}_2 = \angle 0^\circ \text{A}$, $P_1 = 100\text{W}$

9-14 (1) 10H

9-15 $0.395\sqrt{2}\cos(314t - 31.4^\circ)\text{A}$, $1.333\sqrt{2}\cos(314t + 1.1^\circ)\text{A}$

9-16 6.39A, 4.29A, 38.6%

9-17 $(6 - 2e^{-t} - 4e^{-4t})\text{A}$

9-18 $\sqrt{2}\angle -135^\circ \text{V}$

9-19 2, 8W

9-20 2, 1.25W

9-21 $27.95\angle -153.4^\circ \text{V}$

9-22 a) $0.25 + j0.25\Omega$ b) 2.6Ω

9-23 $2\angle -126.87^\circ \text{ A}$

9-24 $\sqrt{2}$, $-j0.5\Omega$, 6.25W

9-25 $\frac{1}{\sqrt{2L_1C_1}}$

第 10 章

10-1 设 $\dot{U}_{AB}=380\angle 0^\circ\text{V}$, 则 $\dot{I}_A=22\angle -66.9^\circ\text{A}$, $\dot{I}_B=22\angle 173.1^\circ\text{A}$, $\dot{I}_C=22\angle 53.1^\circ\text{A}$ 。

10-2 8.2A 。

10-3 (1) 设 $\dot{U}_{AB}=380\angle 0^\circ\text{V}$, 则 $\dot{I}_A=4\angle 39.8^\circ\text{A}$, $\dot{I}_B=4\angle 140.2^\circ\text{A}$, $\dot{I}_C=4\angle 90^\circ\text{A}$,

$\dot{I}_N=9.12\angle 90^\circ\text{A}$;

(2) $\dot{I}_A=10\angle 0^\circ\text{A}$, $\dot{I}_B=10\angle -180^\circ\text{A}$, $\dot{I}_C=4\angle 90^\circ\text{A}$, 550V , 550V , 220V 。

10-4 13.2A , 7.6A 。

10-5 (1) 3.29A , 1.9A , 380V ; (2) 2A , $2\sqrt{3}\text{A}$ 。

10-6 (1) $\frac{10}{3}\sqrt{3}\text{A}$, $\frac{10}{3}\sqrt{3}\text{A}$, 10A ; (2) $5\sqrt{3}\text{A}$, 0 , $5\sqrt{3}\text{A}$; (3) $\frac{10}{3}\sqrt{3}\text{A}$, 0 , $\frac{10}{3}\sqrt{3}\text{A}$ 。

10-7 $\dot{I}_A=51.8\angle -13.63^\circ\text{A}$, $\dot{I}_B=51.8\angle -133.63^\circ\text{A}$, $\dot{I}_C=51.8\angle 106.37^\circ\text{A}$, $\dot{I}_N=0$ 。

10-8 (1) $\dot{I}_A=9.37\angle -41.9^\circ\text{A}$, $\dot{I}_B=9.37\angle -162.9^\circ\text{A}$, $\dot{I}_C=9.37\angle 78.1^\circ\text{A}$;

(2) 0.978

10-9 $\omega L = \frac{1}{\omega C} = \sqrt{3}R$, Y 接法时, $L = 100\text{mH}$, $C = 91.9\mu\text{F}$;

$$\Delta\text{接法时}, \omega L = \frac{1}{\omega C} = \frac{R}{\sqrt{3}}。$$

10-10 (1) 6.64A , 1587W ;

(2) 19.92A , 11.5A , 4761W 。

10-11 3.58A , 1154W 。

10-12 (1) 803W , 1893W ; (2) 1887Var , 0.8192 。

10-13 (1) 设 $\dot{U}_{AN}=220\angle 0^\circ\text{V}$, $\dot{I}_A=3.11\angle -45^\circ\text{A}$, $\dot{I}_B=3.11\angle -165^\circ\text{A}$, $\dot{I}_C=3.11\angle 75^\circ\text{A}$;

(2) $\dot{I}_A=5.47\angle -30.78^\circ\text{A}$, $\dot{I}_B=5.6\angle -179^\circ\text{A}$, $\dot{I}_C=3.11\angle 75^\circ\text{A}$;

(3) 2078.4W, 37.88W。(答案已改)

10-14 17.42kW, 23.2kVar

10-15 (1) 2.787kW, -0.387kW;

(2) 并联Δ接法 C, $Q_C=3.699\text{kVar}$, 1.72kW, 0.68kW。

10-16 $\dot{I}_B=10.53\angle-150^\circ\text{A}$

10-17 (1) 0, 65.82A, 25.6kW;

(2) 40.5A, 65.82A。

第 11 章

11-1 (b); (a)、(d); (d); (b)、(d)

11-3 (a) $\frac{1}{2} + \frac{1}{\pi} \sum_{k=1}^{\infty} \frac{1}{k} \sin \frac{2k\pi}{T} t \quad k=1,2,3\dots$

(b) $\frac{4}{\pi} \sum_{k=1}^{\infty} \frac{1}{k} \sin k\omega t \quad k=1,3,5\dots$

11-4 $5\sqrt{2}\text{A}$, 1.29V

11-5 101.4V, 684.1W

11-6 (1) 10Ω , 31.86mH, 318.3 μF

(2) -99.45°

(3) 515.4W

11-7 $[12.83\cos(10^3t-3.72^\circ)-1.395\sin(2*10^3t-64.3^\circ)]\text{A}$, 9.126A, 916W

11-8 77.14V, 63.63V

11-9 10A

11-10 50V, 2W

11-11 $u_C(t)=20+20\sqrt{2}\cos(10^3t-90^\circ)\text{V}$, 8W

11-12 $i(t)=4.68\cos(\omega t+9.44^\circ)+3\cos(3\omega t-90^\circ)\text{V}$, 3.93A, 27.6V, 92.7W

11-13 (1) $[0.833+1.403\sin(314t+19.32^\circ)-0.941\cos(628t+54.55^\circ)+0.487\sin(942t+71.19^\circ)]\text{A}$

(2) 1.497A, 91.38V

(3) 120W

11-14 $[2.96\sin(3t-52.49^\circ)+0.147\cos(4t+65.54^\circ)]\text{V}$, 2.1V

$$i_1(t) = 1.5 + 0.4\sqrt{2}\cos(\omega t - 90^\circ) + 0.1\sqrt{2}\cos(2\omega t - 90^\circ) \text{ A}, 1.56\text{A}$$

11-15 $i_2(t) = 0.3\sqrt{2}\cos(\omega t - 90^\circ) \text{ A}$, 0.3A

$$u_c(t) = 60 + 30\sqrt{2}\cos(\omega t - 180^\circ) \text{ V}, 67.08\text{V}$$

11-16 $10\mu\text{F}$, $1.25\mu\text{F}$

11-17 1H , $1\mu\text{F}$, $220\sqrt{2}\cos(1000t+30^\circ) \text{ V}$

11-18 $\frac{1}{49\omega^2}\text{H}$, $\frac{1}{9\omega^2}\text{F}$, 或 $\frac{1}{9\omega^2}\text{H}$, $\frac{1}{49\omega^2}\text{F}$

11-19 10Ω , 10mH , 33.3F , 30Ω , $u(t)=15+6\cos(2\times 10^3t+45^\circ) \text{ V}$

第 12 章

12-3 基本回路

(1) (5,1,2,3,4), (6,1,2), (7,1,2,3), (8,2,3,4), (9,2,3), (10,3,4)

(2) (1,5,8), (2,5,6,8), (3,6,7), (4,5,7), (9,5,7,8), (10,5,6)

12-4 (a) 1 2 3 7 4 5 6 8

$$B_f = \begin{bmatrix} 1 & -1 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & -1 & 0 & 0 & 1 & 0 \\ -1 & 0 & -1 & 1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$Q_f = \begin{bmatrix} 1 & 0 & 0 & 0 & -1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 & -1 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & -1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 0 & 1 & -1 \end{bmatrix}$$

12-5

$$Q_f = \begin{bmatrix} -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & 1 & 0 & 0 & 1 \end{bmatrix}$$

12-7

$$B_f = \begin{bmatrix} -1 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & 1 & 0 \\ -1 & -1 & -1 & 1 & 0 & 0 & 1 \end{bmatrix}$$

$$Q_f = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & 1 & -1 \end{bmatrix}$$

12-8

$$\begin{bmatrix} 3 & -1 & -1 & 0 \\ -1 & 2.5 & -1 & -0.5 \\ -1 & -1 & 4 & -1 \\ 0 & -0.5 & -1 & 2.5 \end{bmatrix} \begin{bmatrix} U_{n1} \\ U_{n2} \\ U_{n3} \\ U_{n4} \end{bmatrix} = \begin{bmatrix} 5 \\ -1 \\ -4 \\ 0 \end{bmatrix}$$

12-9

$$Y = \begin{bmatrix} \frac{1}{R_1} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{R_2} & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{\beta}{R_2} & \frac{1}{R_3} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{j\omega L_4} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & j\omega C_5 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & j\omega C_6 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & \frac{1}{R_7} \end{bmatrix} \quad \dot{U}_s = \begin{bmatrix} -\dot{U}_{s1} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \dot{I}_s = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ \dot{I}_{s7} \end{bmatrix}$$

$$\begin{bmatrix} (\frac{1}{R_1} + \frac{1}{R_2} + \frac{\beta}{R_2} + \frac{1}{R_3} + \frac{1}{j\omega L_4}) & -\frac{1}{R_3} & 0 \\ -(\frac{\beta}{R_2} + \frac{1}{R_3}) & (\frac{1}{R_3} + j\omega C_5 + j\omega C_6) & -j\omega C_6 \\ 0 & -j\omega C_6 & \frac{1}{R_7} + j\omega C_6 \end{bmatrix} \begin{bmatrix} \dot{U}_a \\ \dot{U}_b \\ \dot{U}_c \end{bmatrix} = \begin{bmatrix} \frac{\dot{U}_{s1}}{R_1} \\ 0 \\ \dot{I}_{s7} \end{bmatrix}$$

12-10

$$\begin{bmatrix} G_1 + G_2 + G_4 & -G_2 - G_4 + g_{23} \\ -G_2 - G_4 - g_{31} & G_2 + G_3 + G_4 - g_{23} \end{bmatrix} \begin{bmatrix} u_a \\ u_b \end{bmatrix} = \begin{bmatrix} i_{s1} \\ 0 \end{bmatrix}$$

12-11

(2) 设 $\Delta = j\omega(L_5 L_6 - M^2)$

$$\begin{bmatrix} (\frac{1}{R_1} + j\omega C_3 + \frac{L_6}{\Delta}) & -(\frac{L_6+M}{\Delta}) & -j\omega C_3 + \frac{M}{\Delta} \\ -(\frac{L_6+M}{\Delta}) & j\omega C_4 + \frac{L_5+L_6+2M}{\Delta} & -(\frac{L_5+M}{\Delta}) \\ -j\omega C_3 + \frac{M}{\Delta} & -(\frac{L_5+M}{\Delta}) & \frac{L_5}{\Delta} + j\omega C_2 + j\omega C_3 \end{bmatrix} \begin{bmatrix} \dot{U}_{n1} \\ \dot{U}_{n2} \\ \dot{U}_{n3} \end{bmatrix} = \begin{bmatrix} \dot{I}_{s1} \\ 0 \\ j\omega C_2 \dot{U}_{s2} \end{bmatrix}$$

12-12

$$\begin{bmatrix} R_1 + j\omega L_2 & j\omega L_2 & 0 & 0 \\ j\omega L_2 & j\omega L_2 + j\omega L_3 & j\omega M & 0 \\ 0 & j\omega M & j\omega L_4 + \frac{1}{j\omega C_5} & \frac{1}{j\omega C_5} \\ 0 & 0 & \frac{1}{j\omega C_5} & \frac{1}{j\omega C_5} + R_6 \end{bmatrix} \begin{bmatrix} \dot{I}_{l1} \\ \dot{I}_{l2} \\ \dot{I}_{l3} \\ \dot{I}_{l4} \end{bmatrix} = \begin{bmatrix} -\dot{U}_{s1} \\ 0 \\ 0 \\ -R_6 \dot{I}_{s6} \end{bmatrix}$$

12-13

$$\begin{bmatrix} 3 & -2 & 1 & 1 \\ -2 & 5 & -2 & -3 \\ 1 & -2 & 3 & 2 \\ 1 & -3 & 2 & 4 \end{bmatrix} \begin{bmatrix} \dot{I}_{l1} \\ \dot{I}_{l2} \\ \dot{I}_{l3} \\ \dot{I}_{l4} \end{bmatrix} = \begin{bmatrix} 0 \\ -\dot{I}_s \\ \dot{I}_s - \dot{U}_s \\ \dot{I}_s \end{bmatrix}$$

$$\begin{bmatrix} 3 & 2 & 2 & -1 \\ 2 & 4 & 3 & -1 \\ 2 & 3 & 5 & -2 \\ -1 & -1 & -2 & 3 \end{bmatrix} \begin{bmatrix} \dot{U}_{t1} \\ \dot{U}_{t2} \\ \dot{U}_{t3} \\ \dot{U}_{t4} \end{bmatrix} = \begin{bmatrix} 0 \\ \dot{I}_s + \dot{U}_s \\ \dot{U}_s \\ 0 \end{bmatrix}$$

12-14

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{j\omega L_6} + j\omega C_4 & -j\omega C_4 & -\frac{1}{j\omega L_6} \\ -j\omega C_4 & \frac{1}{R_5} + \frac{1}{j\omega L_2} + j\omega C_4 & -\frac{1}{R_5} \\ -\frac{1}{j\omega L_6} & -\frac{1}{R_5} & \frac{1}{R_7} + \frac{1}{R_5} + \frac{1}{j\omega L_6} + j\omega C_3 \end{bmatrix} \begin{bmatrix} \dot{U}_{t1} \\ \dot{U}_{t2} \\ \dot{U}_{t3} \end{bmatrix} = \begin{bmatrix} \frac{\dot{U}_{s1}}{R_1} - \frac{\dot{U}_{s6}}{j\omega L_6} \\ 0 \\ \dot{I}_{s7} + \frac{\dot{U}_{s6}}{j\omega L_6} \end{bmatrix}$$

12-15 (1)

$$\begin{bmatrix} u_C \\ i_L \end{bmatrix} = \begin{bmatrix} -0.25 & -1 \\ 31 & -6 \end{bmatrix} \begin{bmatrix} u_a \\ u_b \end{bmatrix} + \begin{bmatrix} 0.25 \\ -30 \end{bmatrix} u_s$$

12-16 (1)

$$\begin{bmatrix} u_{C1} \\ u_{C2} \\ i_{L1} \\ i_{L2} \end{bmatrix} = \begin{bmatrix} -1 & -1 & 0.5 & -1 \\ -1 & -1 & -0.5 & -1 \\ -0.5 & 0.5 & -0.5 & 0 \\ 0.5 & 0.5 & 0 & 0 \end{bmatrix} \begin{bmatrix} u_{C1} \\ u_{C2} \\ i_{L1} \\ i_{L2} \end{bmatrix} + \begin{bmatrix} 0.5 & 0.5 \\ -0.5 & 0.5 \\ 0.5 & 0.5 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} 2 \cos t \\ 2e^{-t} \end{bmatrix}$$

12-17

$$\begin{bmatrix} u_{C1} \\ u_{C2} \\ i_{L1} \end{bmatrix} = \begin{bmatrix} -\frac{1}{3} & 0 & -\frac{1}{3} \\ 0 & -\frac{1}{6} & \frac{1}{2} \\ \frac{2}{3} & -1 & -\frac{2}{3} \end{bmatrix} \begin{bmatrix} u_{C1} \\ u_{C2} \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{3} & -\frac{1}{3} \\ 0 & -\frac{1}{6} \\ \frac{1}{3} & -\frac{1}{3} \end{bmatrix} \begin{bmatrix} u_{s1} \\ u_{s2} \end{bmatrix}$$

12-18

$$\begin{bmatrix} u_{C1} \\ u_{C2} \\ i_L \end{bmatrix} = \begin{bmatrix} -1 & 0 & 1 \\ 0 & -0.5 & -1 \\ -1 & -3 & 0 \end{bmatrix} \begin{bmatrix} u_{C1} \\ u_{C2} \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ 0.5 \\ 2 \end{bmatrix} u_{s1}$$

第13章

$$13-1 \quad \text{a)} \quad \frac{1}{11} \begin{bmatrix} 5 & 5 \\ 5 & 5 \end{bmatrix} \Omega \quad \text{b)} \quad \begin{bmatrix} 6 & 2 \\ 4 & 5 \end{bmatrix} \Omega$$

$$13-2 \quad \text{a)} \quad \begin{bmatrix} 0.4 & -0.2 \\ -0.2 & 1.2 \end{bmatrix} \text{S} \quad \text{b)} \quad \begin{bmatrix} \frac{1}{8} & -\frac{1}{28} \\ 0 & \frac{1}{7} \end{bmatrix} \text{S}$$

$$13-3 \quad \text{a)} \quad \begin{bmatrix} \frac{4}{15} & \frac{13}{4} \\ \frac{13}{4} & \frac{15}{4} \end{bmatrix} \Omega \quad \begin{bmatrix} \frac{15}{14} & -\frac{13}{14} \\ -\frac{13}{14} & \frac{15}{14} \end{bmatrix} S$$

$$\text{b)} \quad \begin{bmatrix} \frac{3}{8} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{3}{8} \end{bmatrix} \Omega \quad \begin{bmatrix} 3 & 1 \\ 1 & 3 \end{bmatrix} S$$

$$13-4 \quad \text{a)} \quad T = \begin{bmatrix} \frac{L_1}{M} & j\omega \frac{L_1 L_2 - M^2}{M} \\ 1 & \frac{L_2}{M} \\ j\omega M & M \end{bmatrix} \quad H = \begin{bmatrix} j\omega \frac{L_1 L_2 - M^2}{L^2} & \frac{M}{L^2} \\ -\frac{M}{L^2} & \frac{1}{j\omega L_2} \end{bmatrix}$$

$$\text{(b)} \quad T = \begin{bmatrix} 2 & 0.5\Omega \\ 1s & 0.75 \end{bmatrix} \quad H = \begin{bmatrix} \frac{2}{3}\Omega & \frac{4}{3} \\ -\frac{4}{3} & \frac{4}{3}s \end{bmatrix}$$

$$13-5 \quad 8\Omega, 6\Omega, 2\Omega, 4\Omega$$

$$13-6 \quad (1) \quad 0.1s, 0.2s, 0.1s \quad (2) \quad \text{含VCCS } 5U_1 \quad 3s, 3s, 2s$$

$$13-7 \quad \frac{1}{3}\Omega, \frac{1}{9}\Omega, \frac{2}{3}\Omega; 2s, 0.333s, 1s$$

$$13-8 \quad \begin{bmatrix} \frac{42}{31} & -\frac{8}{21} \\ -\frac{8}{21} & \frac{17}{21} \end{bmatrix} S$$

$$13-9 \quad \frac{2}{3}\Omega, \frac{1}{3}\Omega, \frac{1}{9}\Omega; 1s, 2s, \frac{1}{3}s$$

$$13-10 \quad \text{a)} \quad R_1, R_1, \frac{R_2 - R_1}{2} \quad \text{b)} \quad \frac{1}{j2\omega C}, -\frac{1}{j4\omega C}, \frac{1}{j2\omega C}$$

$$13-11 \quad R = 3\Omega$$

$$13-12 \quad \frac{12}{19}$$

$$13-13 \quad -\frac{5}{17}$$

$$13-14 \quad Z = Z_{22} - \frac{Z_{12}Z_{21}}{Z_{11}}, \dot{I}_s = \frac{Z_{21}}{Z_{22}Z_{11} - Z_{12}Z_{21}} \dot{U}_1$$

$$13-15 \quad \dot{I}_C = \frac{Z_a \dot{I}_2}{Z_1}, \dot{U}_C = Z_b \dot{I}_1$$

$$13-16 \quad Z_L = 50\Omega, 1W$$

$$13-17 \quad 2\Omega, 12.5W$$

$$13-18 \quad a) \sqrt{\frac{L}{C} - \frac{\omega^2 L^2}{4}} \quad b) \sqrt{\frac{4\omega^2 L^2}{4\omega^2 LC - 1}}$$

$$c) \sqrt{Z_1 Z_2} \quad b) Z_1$$

$$13-19 \quad a) \begin{bmatrix} A & B \\ AY+C & BY+D \end{bmatrix} \quad b) \begin{bmatrix} A & AZ+B \\ C & CZ+D \end{bmatrix}$$

$$13-20 \quad Y = \begin{bmatrix} \frac{5}{2} & -\frac{3}{2} \\ -\frac{3}{2} & \frac{3}{2} \end{bmatrix} S$$

$$13-21 \quad a) \begin{bmatrix} 3.25 & j27\Omega \\ j0.025S & 0.1 \end{bmatrix} \quad b) \begin{bmatrix} 7 & 12\Omega \\ 4S & 7 \end{bmatrix}$$

$$13-22 \quad n = g_2 / g_1$$

$$13-23$$

$$T = \begin{bmatrix} -\frac{1}{gnR} & -\frac{1}{gn} \\ gn & 0 \end{bmatrix} \quad Y = \begin{bmatrix} 0 & gn \\ gn & \frac{1}{R} \end{bmatrix}$$

第 14 章

$$14-1 \quad u = k(8i^4 - 8i^2 + 1)$$

$$14-2 \quad (1) u_1 = 20.8V, u_2 = 20\sin t + 0.8\sin^3 t = (20.6\sin t - 0.2\sin 3t)V$$

$$(2) u \neq u_1 + u_2, u \neq ku_1$$

$$14-3 \quad u_2 = 0.137V, i_2 = 0.04185A$$

$$\text{或 } u_2 = -7.652V, i_2 = 0.0465A$$

$$14-4 \quad 10.828V, \text{ 或 } 5.172V$$

$$14-5 \quad 10^{-6} e^{40u_d} + u_d - 1 - 10^{-6} = 0$$

14-6 3V, 1.5A

14-7 1V, 1.5A

14-8 1A, 1V; -2A, 4V

14-9 20V, 68V

14-14 $\frac{1}{3}\Omega$ 电阻并联 3A 电流源后再并联理想二极管

14-15 2V, 0.5A

14-16 2.45V, 1.73A,

第 15 章

15-1 a) $\frac{E_m \omega (1 + e^{-T_s/2})}{s^2 + \omega^2}$ b) $\frac{E_m \omega}{s^2 + \omega^2} \frac{1}{1 - e^{-T_s/2}}$

c) $\frac{E_m \omega}{s^2 + \omega^2} \cdot \frac{1 + e^{-T_s/2}}{1 - e^{-T_s/2}}$ d) $\frac{e^{-s} - e^{-3s}}{s}$

e) $\frac{1}{s} \frac{1 - e^{-2s}}{1 - e^{-T_s}}$ f) $\frac{se^{-s} + e^{-2s} - e^{-3s}}{s}$

15-2 (1) $\frac{2}{s^3}$ (2) $\frac{a^2}{s^2(s+a)}$ (3) $\frac{a}{s^2 - a^2}$ (4) $\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$

(5) $\frac{2s^2 + 2s + 1}{s^2}$ (6) $\frac{s^2 - a^2}{(s^2 + a^2)^2}$ (7) $\frac{3e^{-5s}}{(s+2)^2}$

(8) $\frac{6e^{-5s}}{s-a}$ (9) $\frac{1 + e^{-s} + e^{-2s} + se^{-2s}}{s+1}$

15-3 (1) $e^{-t} + 3e^{-3t} - 4e^{-4t}$ (2) $4 - 6e^{-250t}$

(3) $2\delta(t) + 5e^{-t} - 5e^{-2t}$ (4) $\frac{1}{4}(1 + 2e^{-2t} + e^{-4t})$

(5) $\frac{3}{8} + \frac{1}{4}\cos\sqrt{2}t + \frac{3}{8}\cos 2t$ (6) $\frac{1}{4} - \frac{1}{4}e^{-2t} + \frac{1}{2} + e^{-2t}$

(7) $50e^{-t} \sin t$ (8) $1 + 5e^{-t} \cos(2t - 53.13^\circ)$

(9) $e^{-t} - (t+1)e^{-2t}$ (10) $\cos ht - 0.5t^2 - 1$

(11) $0.5t \sin t$ (12) $10e^{-2t} - 5e^{-t}$

15-6 a) $\frac{30s^2 + 14s + 1}{6s^2 + 12s + 1}$ b) $\frac{6}{s+9}$ c) $\frac{4s+1}{s+1}$ d) $\frac{5s+1}{4s+1}$

$$\text{e) } \frac{s^2 + 100s + 1000}{s + 100} \quad \text{f) } \frac{s + 1}{s^2 + 2s + 2} \quad \text{g) } \frac{8s + 3}{3s + 1}$$

$$15-7 \quad \infty, 3$$

$$15-8 \quad \text{a) } \frac{8}{3}\varepsilon(t)A - \frac{2}{3}e^{-\frac{3}{2}t}\varepsilon(t)A \quad \text{b) } -\frac{1}{5}e^{-\frac{5}{4}t}\varepsilon(t)A + \frac{1}{5}\varepsilon(t)A$$

$$15-9 \quad \text{a) } 0.156\delta(t)\text{mA} \quad \text{b) } \frac{C_1 U_s}{C_1 + C_2} e^{-\frac{t}{R(C_1 + C_2)}}$$

$$15-10 \quad \text{a) } -\frac{1}{7}e^{-\frac{15}{7}t}A, \frac{1}{7}e^{-\frac{15}{7}t}A; \quad \text{b) } \left(\frac{50}{3} - \frac{5}{3}e^{-1.5t}\right)A; \quad \text{c) } (2 + 1.75e^{-12.5t})A$$

$$15-11$$

$$u_C(t) = 2(1 - e^{-t})\varepsilon(t)V$$

$$15-12 \quad 15(t + 1 - e^{-0.5t})A$$

$$15-13 \quad (10 - 4e^{-\frac{3}{5}t})V$$

$$15-14 \quad \left[10 + 8\sqrt{15}e^{-25t}\sin(25\sqrt{15}t)\right]A$$

$$15-15 \quad \frac{-5(s+1)^2}{s^2(5s+3)}, \frac{25(s+1)^2}{s(11s^2+15s+6)}$$

$$15-16 \quad \frac{5}{2}t - \frac{15}{4} + 7.56e^{-\frac{3}{4}t}\cos\left(\frac{\sqrt{7}}{4}t - 7.18^\circ\right)$$

$$15-17 \quad 32te^{-2t}\varepsilon(t)V$$

$$15-18 \quad [-17.926e^{-50t} + 17.89\sin(\omega t - 63.43^\circ)]V$$

$$15-19 \quad [11.43e^{-0.0357t}\varepsilon(t) - 11.43e^{-0.0357(t-10^{-3})}\varepsilon(t-10^{-3})]V$$

$$15-20 \quad [1 - (1 + 2t)e^{-2t}]\varepsilon(t)V$$

$$15-21 \quad [8.2e^{-3t}\cos(4t + 52.43^\circ) + 2\sin 5t]\varepsilon(t)A$$

$$15-22 \quad [(1 - e^{-\frac{t}{6}})\varepsilon(t) + (1 - e^{-\frac{t-1}{6}})\varepsilon(t-1) - 2(1 - e^{-\frac{t-2}{6}})\varepsilon(t-2)]A$$

$$15-23 \quad 20(e^{-t} - e^{-2t})V, 25\sqrt{25}\sin\sqrt{2}tV$$

$$15-24 \quad u_2(t) = 1V \quad -\infty < t < 0; \quad u_2(t) = (1 - \frac{1}{3}e^{-\frac{4}{3}t})V \quad 0 \leq t < +\infty$$

$$15-25 \quad i_2(t) = [\frac{5}{3}\delta(t) + \frac{5}{18}e^{-\frac{1}{3}t}\varepsilon(t)]A; \quad u_2(t) = (5 - \frac{5}{3}e^{-\frac{1}{3}t})\varepsilon(t)V$$

$$15-26 \quad \frac{U_2(s)}{U_1(s)} = \frac{s}{(s+1)^2 + 2}$$

15-27 $L = 1\text{H}$ 与 $R_1 = 2\Omega$ 串联后在与 $R_2 = \frac{1}{2}\Omega$ 与 $C = 1\text{F}$ 并联后的电路相串联;

$$Z(s) = \frac{1}{s+2} + s + 2$$

15-28 $R_1 C_1 = R_2 C_2$

15-29 设 $a = \frac{1}{RC}$, $H(s) = \frac{s-a}{s+a}$

15-30 $\frac{2}{s+2}$

15-31 $\frac{s(s^2+1.5)}{s^2+1}$

15-32 $I(s) = \frac{2}{s^2+1}$; 极点 $p_{1,2} = \pm j1$

15-34 $\frac{2}{s^2+s+1}$; $\frac{4}{\sqrt{3}} e^{-\frac{t}{2}} \sin \frac{\sqrt{3}}{2} t \varepsilon(t) \text{V}$

15-35

$$Y(s) = \begin{bmatrix} s+2 & -3 \\ -3 & s+5 \end{bmatrix}$$

15-36 $(1000 + \frac{1}{7} \cos 500t) \text{mA}$

$$i(t) = 0.4e^{-0.2t} \text{A} \quad t \geq 0$$